

Amrita Vishwa Vidyapeetham
Amrita School of Engineering, Bangalore
Department of Computer Science and Engineering

19CSE211 Computer Organization and Architecture
Lab Handout - 2
Basic Gates

Exercise Problems

1. Write a verilog code to implement AND gate in gate level modeling

```
module and_g1(a, b, c);  
input a, b;  
output c;  
and a1(c,a,b);  
endmodule
```

```
module and1_tb;  
reg a, b;  
wire c;  
  
and_g1 i(a, b, c);  
  
initial  
begin  
    a=1'b0;  
    b=1'b0;  
    $monitor("Time:%0t a=%b  
b=%b c=%b", $time, a, b, c);  
    #5 a=1'b0; b=1'b0;  
    #5 a=1'b0; b=1'b1;  
    #5 a=1'b1; b=1'b0;  
    #5 a=1'b1; b=1'b1;  
end  
endmodule
```

2. Write a verilog code to implement AND gate in data flow modeling

```
module and_d1(a, b, c);
input a, b;
output c;
assign c = a & b;
endmodule
```

```
module and1_tb;
reg a, b;
wire c;

and_d1 i(a, b, c);

initial
begin
    a=1'b0;
    b=1'b0;
    $monitor("Time:%0t a=%b
b=%b c=%b", $time, a, b, c);
    #5 a=1'b0; b=1'b0;
    #5 a=1'b0; b=1'b1;
    #5 a=1'b1; b=1'b0;
    #5 a=1'b1; b=1'b1;
end
endmodule
```

3. Write a verilog code to implement AND gate in behavioral modeling

```
module and_b1(a, b, c);
input a, b;
output c;
reg c;

always@(a or b or c)
begin
    if(a==1'b1 && b==1'b1)
        c = 1'b1;
    else
        c = 1'b0;
end
endmodule
```

```
module and1_tb;
reg a, b;
wire c;

and_b1 i(a, b, c);

initial
begin
    a=1'b0;
    b=1'b0;
    $monitor("Time:%0t a=%b
b=%b c=%b", $time, a, b, c);
    #5 a=1'b0; b=1'b0;
    #5 a=1'b0; b=1'b1;
    #5 a=1'b1; b=1'b0;
    #5 a=1'b1; b=1'b1;
end
endmodule
```

4. Write a verilog code to implement 5 inputs AND gate in gate level modeling


```
module and_5in(in1, in2, in3, in4, in5, out);
input in1, in2, in3, in4, in5;
output out;
and a1(out, in1, in2, in3, in4, in5);
endmodule

module and1_tb;
reg in1, in2, in3, in4, in5;
wire out;

and_5in i(in1, in2, in3, in4, in5, out);

initial
begin
    in1=1'b0; in2=1'b0;
    in3=1'b0; in4=1'b0; in5=1'b0;
    $monitor("Time:%0t in=%b%b%b%b%b out=%b", $time,
    in1, in2, in3, in4, in5, out);
    #5 in1=1'b0; in2=1'b0;
    in3=1'b0; in4=1'b0; in5=1'b0;
    #5 in1=1'b0; in2=1'b0;
    in3=1'b1; in4=1'b0; in5=1'b1;
    #5 in1=1'b1; in2=1'b1;
    in3=1'b1; in4=1'b1; in5=1'b1;
end
endmodule
```

 5. Write a verilog code to implement below logic circuit using gate level modeling



```
module exp5(a,b,c,x);  
input a, b, c;  
output x;  
wire w1, w2;
```

```
not n1(w1, a);  
or o1(w2, b,c);  
nand n2(x, w1, w2);
```

```
endmodule
```

```
module exp5_tb;
```

```
reg a, b, c;  
wire x;
```

```
exp5 i(a, b, c, x);
```

```
initial  
begin
```

```
    a = 1'b0;
```

```
    b = 1'b0;
```

```
    c = 1'b0;
```

```
    $monitor("Time:%0t a=%b  
b=%b, c=%b, x=%b", $time, a, b,  
c, x);
```

```
    #5 a= 1'b0; b=1'b0; c=1'b0;
```

```
    #5 a= 1'b0; b=1'b0; c=1'b1;
```

```
    #5 a= 1'b0; b=1'b1; c=1'b0;
```

```
    #5 a= 1'b0; b=1'b1; c=1'b1;
```

```
    #5 a= 1'b1; b=1'b0; c=1'b0;
```

```
    #5 a= 1'b1; b=1'b0; c=1'b1;
```

```
    #5 a= 1'b1; b=1'b1; c=1'b0;
```

```
    #5 a= 1'b1; b=1'b1; c=1'b1;
```

```
end
```

```
endmodule
```

Assignment

1. Write a verilog code to implement following gate in data flow level modeling
 - a. OR
 - b. NAND
 - c. EXOR (XOR)
2. Write a verilog code to implement the below logic circuit using gate level and data flow modeling

