 


Amrita Vishwa Vidyapeetham
Amrita School of Computing, Bangalore
Department of Computer Science and Engineering
19CSE211 Computer Organization and Architecture
Lab Handout - 5
Sequential Circuits
Counters and Shift Registers

Exercise Problems

1. Write a verilog code to implement 3 bit asynchronous counter using T flip-flop



```
module tff(T, clk, Q, reset);
```

```
input T, clk, reset;
```

```
output Q;
```

```
reg Q;
```

```
always @(posedge clk)
```

```
begin
```

```
    if (reset)
```

```
        Q = 0;
```

```
    else begin
```

```
        if(T)
```

```
            Q = ~Q;
```

```
        else
```

```
            Q = Q;
```

```
    end
```

```
end
```

```
endmodule
```

```
module a_counter_3(T, Q, clk,  
reset);
```

```
input [2:0] T;
```

```
input clk, reset;
```

```
output [2:0] Q;
```

```
tff i1(T[0], clk, Q[0], reset);
```

```
tff i2(T[1], ~Q[0], Q[1], reset);
```

```
tff i3(T[2], ~Q[1], Q[2], reset);
```

```
endmodule
```

```
module a_counter_3_tb;
```

```
reg [2:0] T;
```

```
reg clk, reset;
```

```
wire [2:0] Q;
```

```
a_counter_3 i1(T, Q, clk, reset);
```

```
always #5 clk = ~clk;
```

```
initial
```

```
begin
```

```
    T = 3'b000; reset = 1; clk = 1'b0;
```

```
    $monitor("Time=%f, T=%3b, clk=%b, Q=%3b",  
$time, T, clk, Q);
```

```
    #10 reset = 0;
```

```
    #10 T=3'b111;
```


```
    #80 $finish;
```

```
end
```

```
endmodule
```

2. Write a verilog code to implement 3-bit Johnson counter

Q _A	Q _B	Q _C	Q _D
0	0	0	0
1	0	0	0
1	1	0	0
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
repeat			

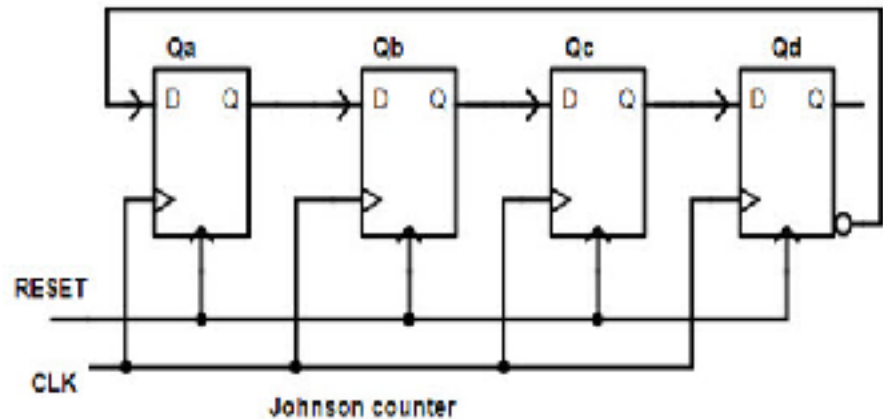

```

module dff(D, clk, Q, reset);
    input D, clk, reset;
    output Q;
    reg Q;

    always @(posedge clk)
        if (reset) begin
            Q = 0;
        end
        else begin
            Q = D;
        end
endmodule

module johnson_counter(reset,
    clk, Q);

    input reset, clk;
    output [3:0] Q;

    dff i1(~Q[0], clk, Q[3],
        reset);
    dff i2(Q[3], clk, Q[2], reset);
    dff i3(Q[2], clk, Q[1], reset);
    dff i4(Q[1], clk, Q[0], reset);

endmodule

module johnson_counter_tb;
    reg reset, clk;
    wire [3:0] Q;


    johnson_counter i(reset, clk, Q);

    always #5 clk = ~clk;

    initial
        begin
            clk=1'b0; reset=1'b1;
            $monitor("Time:%f, clk=%b,
                Q=%4b", $time, clk, Q);
            #10 reset = 1'b0;
            #100 $finish;
        end
endmodule

```

 3. Write a verilog code to implement 4 bit Serial In Serial Out shift registers



```

module dff(D, clk, Q);
    input D, clk;
    output Q;
    reg Q;

    always @(posedge clk)
        begin
            Q = D;
        end
endmodule

module siso(in, out, clk);
    input in, clk;
    output out;
    wire [2:0] Q;

    dff i1(in, clk, Q[0]);
    dff i2(Q[0], clk, Q[1]);
    dff i3(Q[1], clk, Q[2]);
    dff i4(Q[2], clk, out);
endmodule

module siso_tb;
    reg in, clk;
    wire out;


    siso i(in, out, clk);

    always #5 clk = ~clk;

    initial
        begin
            in = 1'b0; clk = 1'b0;
            $monitor("Time:%f, in:%b, clk:
            %b, out:%b", $time, in, clk, out);
            #10 in = 1'b1;
            #10 in = 1'b0;
            #10 in = 1'b1;
            #10 in = 1'b0;
            #60 $finish;
        end
endmodule

```

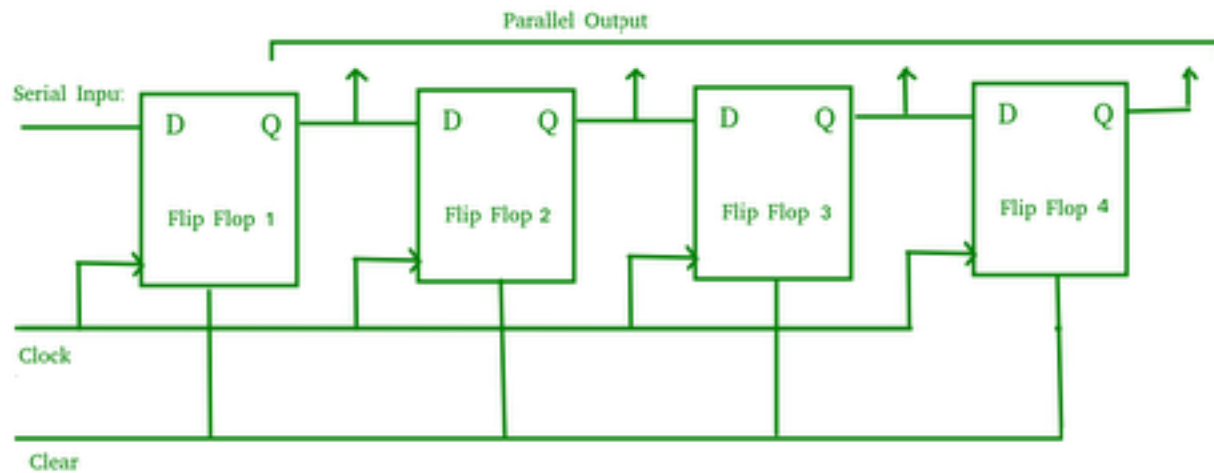4. Write a verilog code to implement 4 bit Serial In parallel Out shift registers



```
module dff(D, clk, Q);
```

```
input D, clk;
```

```
output Q;
```

```
reg Q;
```

```
always @(posedge clk)
```

```
begin
```

```
    Q = D;
```

```
end
```

```
endmodule
```

```
module sipo(in, out, clk);
```

```
input in, clk;
```

```
output [3:0] out;
```

```
dff i1(in, clk, out[0]);
```

```
dff i2(out[0], clk, out[1]);
```

```
dff i3(out[1], clk, out[2]);
```

```
dff i4(out[2], clk, out[3]);
```

```
endmodule
```

```
module sipo_tb;
```

```
reg in, clk;
```

```
wire [3:0] out;
```

```
sipo i(in, out, clk);
```

```
always #5 clk = ~clk;
```

```
initial
```

```
begin
```

```
    in = 1'b0; clk = 1'b0;
```

```
    $monitor("Time:%f, in:%b,
```

```
    clk:%b, out:%4b", $time, in, clk,
```

```
    out);
```

```
    #10 in = 1'b1;
```

```
    #10 in = 1'b0;
```

```
    #10 in = 1'b1;
```

```
    #10 in = 1'b0;
```

```
    #60 $finish;
```


```
end
```

```
endmodule
```

Assignment

 1. Write a verilog code to implement 3-bit Ring counter.

Hint: Preset signal should be added in the D flip flop module



2. Write a verilog code to implement 4 bit parallel In parallel Out shift registers

